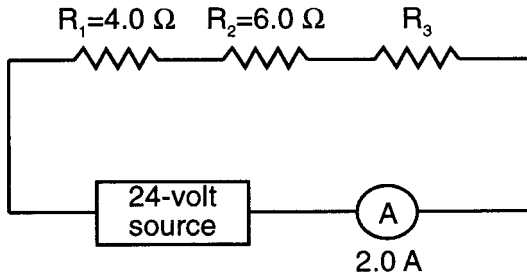


Circuits (R)


1. A student needs a 4-ohm resistor to complete a circuit. Only a large quantity of 1-ohm resistors are available. Which of the following should be done to complete the circuit?
 - 1) Connect four 1-ohm resistors in series.
 - 2) Connect four 1-ohm resistors in parallel.
 - 3) Connect two of the 1-ohm resistors in series and two in parallel.
 - 4) Connect only two 1-ohm resistors in parallel.

2. The diagram below shows a circuit with three resistors.



What is the resistance of resistor R_3 ?

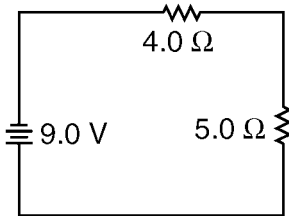
- 1) 6.0 Ω
 - 2) 2.0 Ω
 - 3) 12 Ω
 - 4) 4.0 Ω
3. A 9.0-volt battery is connected to a 4.0-ohm resistor and a 5.0-ohm resistor as shown in the diagram below.



What is the current in the 5.0-ohm resistor?

- 1) 1.0 A
- 2) 2.3 A
- 3) 1.8 A
- 4) 4.0 A

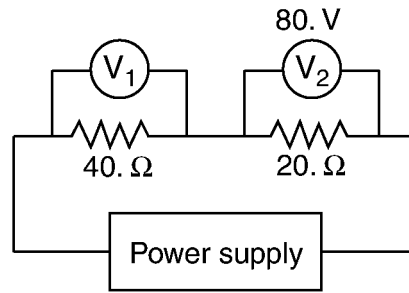4. In the circuit shown below, voltmeter V_2 reads 80. volts.




What is the reading of voltmeter V_1 ?

- 1) 160 V
 - 2) 80. V
 - 3) 40. V
 - 4) 20. V
5. A 100.-ohm resistor and an unknown resistor are connected in series to a 10.0-volt battery. If the potential drop across the 100.-ohm resistor is 4.00 volts, the resistance of the unknown resistor is

- 1) 50 Ω
- 2) 100 Ω
- 3) 150 Ω
- 4) 200 Ω

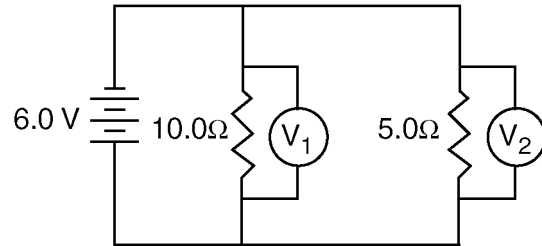
6. In the circuit diagram below, what are the correct readings of voltmeters V_1 and V_2 ?



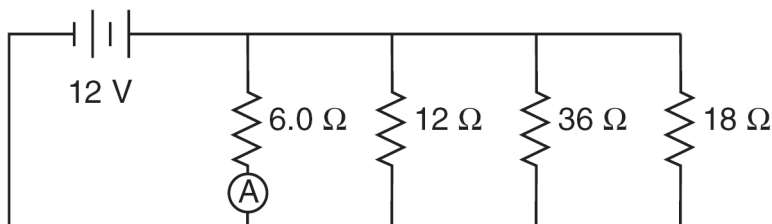- 1) V_1 reads 2.0 V and V_2 reads 4.0 V
- 2) V_1 reads 4.0 V and V_2 reads 2.0 V
- 3) V_1 reads 3.0 V and V_2 reads 3.0 V
- 4) V_1 reads 6.0 V and V_2 reads 6.0 V


Circuits (R)

Base your answers to questions 7 and 8 on the diagram below, which represents an electric circuit consisting of four resistors and a 12-volt battery.



7. What is the equivalent resistance of this circuit?
 1) 72 Ω 2) 18 Ω 3) 3.0 Ω 4) 0.33 Ω
8. How much power is dissipated in the 36-ohm resistor?
 1) 110 W 2) 48 W 3) 3.0 W 4) 4.0 W

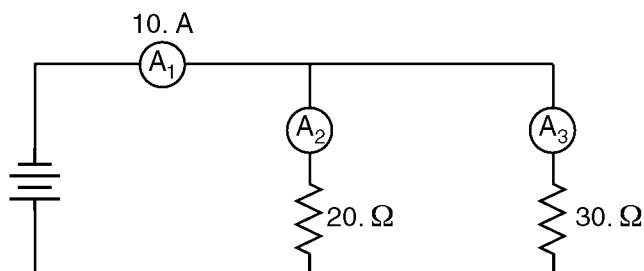
9. What is the total current in a circuit consisting of six operating 100-watt lamps connected in parallel to a 120-volt source?
 1) 5 A 3) 600 A
 2) 20 A 4) 12 000 A
10. In the circuit diagram shown below, ammeter A_1 reads 10. amperes.




What is the reading of ammeter A_2 ?

- 1) 6.0 A 3) 20. A
 2) 10. A 4) 4.0 A
11. As the number of resistors in a parallel circuit is increased, what happens to the equivalent resistance of the circuit and total current in the circuit?
- 1) Both equivalent resistance and total current decrease.
 - 2) Both equivalent resistance and total current increase.
 - 3) Equivalent resistance decreases and total current increases.
 - 4) Equivalent resistance increases and total current decreases.

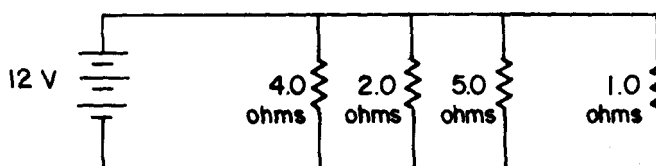12. In the circuit diagram shown below, what is the current through the 4.0-ohm resistor?



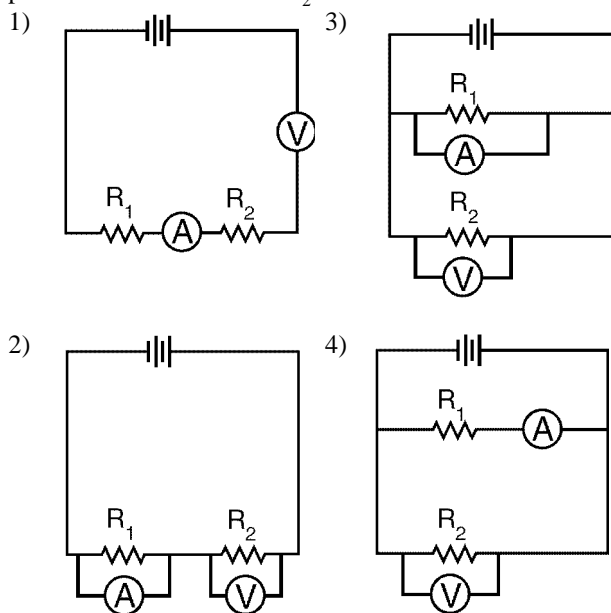- 1) 1.0 ampere 3) 3.0 amperes
 2) 0.33 ampere 4) 48 amperes
13. In which circuit represented below are meters properly connected to measure the current through resistor R_1 and the potential difference across R_2 ?



14. One watt is equivalent to one
 1) $\text{N}\cdot\text{m}$ 3) $\text{J}\cdot\text{s}$
 2) N/m 4) J/s

Circuits (R)

15. A microwave oven operating at 120 volts is used to heat a hot dog. If the oven draws 12.5 amperes of current for 45 seconds, what is the power dissipated by the oven?

- | | |
|------------------------|------------------------|
| 1) 33 W | 3) 5.4×10^3 W |
| 2) 1.5×10^3 W | 4) 6.8×10^4 W |

16. A device operating at a potential difference of 1.5 volts draws a current of 0.20 ampere. How much energy is used by the device in 60. seconds?

- | | |
|----------|---------|
| 1) 4.5 J | 3) 12 J |
| 2) 8.0 J | 4) 18 J |

Circuits (R)
Answer Key
[New Exam]

1. 1

2. 2

3. 1

4. 1

5. 3

6. 4

7. 3

8. 4

9. 1

10. 1

11. 3

12. 3

13. 4

14. 4

15. 2

16. 4
